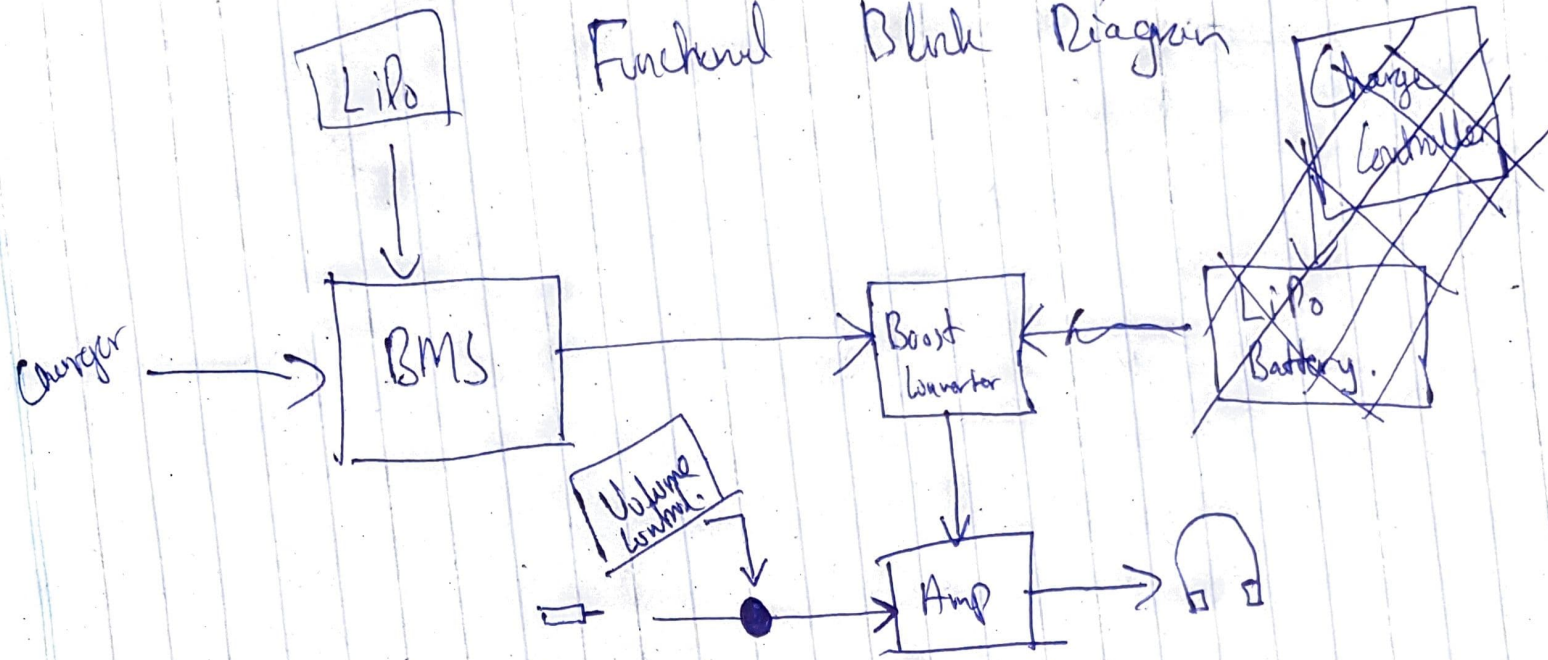


Functional Block Diagram



BMS:

- Short Circuit
- Over Discharge
- Over Charge
- Charging Management

Boost Converter (TPS6103)

$$\frac{0.49}{0.153125} = \frac{3.2(V)}{1}$$

$$\frac{0.49}{3.2} = \frac{R_2}{R_1 + R_2}$$

390k, 60k.

$$0.49 = 3.2 \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\frac{0.49}{3.2} (R_1 + R_2) = R_2$$

$$0.153125(R_2) - R_2 = -0.153125 R_1$$

$$R_2 - 0.153125(R_2) = 0.153125 R_1, \text{ for } \boxed{R_2 = 100k}$$

$$\boxed{R_1 = 553k\Omega}$$

$$R_4 = 180k\Omega$$

$$R_5 = 1.62M\Omega$$

$$\boxed{R_6 = 1M\Omega \leftarrow \text{Pullup.}}$$

$$C_{in} = 10\mu F$$

$$+ 100nF \leftarrow \text{Ceramic / Tantalum.}$$

$$C_{out} = 220\mu F \leftarrow \text{low ESR } < 30m\Omega$$

$$+$$

$$2.2\mu F \leftarrow \text{low ESR } < 30m\Omega$$

$$I = 6.8A \leftarrow 4A \text{ rated. low ESR.}$$

Audio Amplifier (TPA 6112 AC)

Differential Audio Amplifier Configuration

Gain $\leftarrow 10$

$R_f = 10k$
 $R_i = 1k$ } Metal Film Resistors.

$$C_1 \neq \frac{1}{2\pi(1000)(20)}$$

$C_1 \leq 8.0\mu F$

\leftarrow Low leakage
Tantalum / Ceramic Capacitors.

$C_s = 0.1\mu F \leftarrow$ Low ESR ceramic
 $+ 10\mu F \leftarrow$ Electrolyte Aluminium.

~~$R_B = 10k$~~

$C_B = 1\mu F \leftarrow$ Low ESR Ceramic/
Tantalum

$C_c = 220\mu F \leftarrow$ Low ESR
Tantalum / Ceramic.

BMS

Refer to GreatBattery Video.

- Charge Controller
- Battery Protection - PMIC.

Protection Circuit (FS312F-G)

- Use Typical Application Circuit.

Battery Charger (BQ21040)

- Use Simplified Schematic
- Set $R_{\text{ISET}} = 675 \Omega$